
Name- Ashakuzzaman Odree Id-20301268 Section-06 Serial number-26 Lab-4

```
#Task-2
module lab(Clock, Reset, w, z,y,Y);
input Clock, Reset, w;
output reg z;
output reg [1:0] y,Y;
parameter [1:0] A = 0, B = 1, C = 2;
always @(posedge Clock, posedge Reset)
begin
if (Reset == 1)
begin
y = 0;
Y=0;
z=0;
end
else
begin
y=Y;
case(y)
A: if (w)
begin
Y = A;
z=0;
end
else
begin
Y= B;
z=0;
```

```
end
B: if (w)
begin
Y= C;
z=0;
end
else
begin
Y= B;
z=0;
end
C: if (w)
begin
Y= A;
z=0;
end
else
begin
Y= B;
z=1;
end
default: Y = 2'bxx;
endcase
end
end
endmodule
```

 

Problem 2:

Suppose that we wish to design a Mealy type Finite State Machine (FSM) that meets the following specification:

- The FSM has one input w, and one output z.
- All changes in the FSM occur on the positive edge of a clock signal.
- The FSM has reset functionality.
- FSM will generate z = 1 at the instant the input values of w has the pattern:

=> 010

[Overlapping of the input patterns should be detected]

